

**HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY
FACULTY OF ELECTRICAL AND ELECTRONIC
ENGINEERING**



[DIGITAL SYSTEM]

Instructor/ Lecturer: Ms. Phan Vo Kim Anh

Class/Group: TT04

Name:

Nguyễn Vũ Thanh Tùng

Nguyễn Doãn Khải

Student ID:

2051024

2010332

REPORT LAB 6

PROJECT

A/ VHDL CODE FOR LAB 6:

I) VHDL code describing simple elements in the circuit:

1. REGISTER:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY regn IS
generic (n: natural:= 9);
PORT (      D : IN STD_LOGIC_VECTOR(n-1 downto 0);
        Clk, Reset, Load :IN STD_LOGIC;
        Q : OUT STD_LOGIC_VECTOR(n-1 downto 0));
END regn;
ARCHITECTURE behavioral OF regn IS
BEGIN
PROCESS (Clk, Reset)
BEGIN
    IF (Reset = '0') THEN
        Q <= (others => '0');
    ELSIF Load = '1' AND rising_edge(Clk) THEN
        Q <= D;
    END IF;
END PROCESS;
END behavioral;
```

2.7 SEGMENT HEX:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY my_7seghex IS
PORT (      C: IN STD_LOGIC_VECTOR(3 DOWNT0 0);
        Z : OUT STD_LOGIC_VECTOR(0 TO 6));
END my_7seghex;

ARCHITECTURE dataflow OF my_7seghex IS
BEGIN
With C select
Z <=  NOT "1111110" when "0000",
      NOT "0110000" when "0001",
      NOT "1101101" when "0010",
      NOT "1111001" when "0011",
      NOT "0110011" when "0100",
      NOT "1011011" when "0101",
      NOT "1011111" when "0110",
      NOT "1110000" when "0111",
      NOT "1111111" when "1000",
      NOT "1111011" when "1001",
      NOT "1110111" when "1010",
      NOT "0011111" when "1011",
      NOT "1001110" when "1100",
      NOT "0111101" when "1101",
      NOT "1001111" when "1110",
      NOT "1000111" when "1111",
      NOT "0000000" when OTHERS;
END dataflow;
```

3.D FLIP FLOP POSITIVE EDGE:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY minedFFpositive_edge IS
PORT (D, Clk, RESET : IN STD_LOGIC;
      Q : OUT STD_LOGIC);
END minedFFpositive_edge;

ARCHITECTURE behavior OF minedFFpositive_edge IS
BEGIN
PROCESS (Clk, Reset)
BEGIN
    IF (Reset = '0') THEN
        Q <= '0';
    ELSIF rising_edge(Clk) THEN
        Q <= D;
    END IF;
END PROCESS;
END behavior;
```

4.DECODER 3 TO 8:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY dec3to8 IS
PORT (      W : IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      En : IN STD_LOGIC;
      Y : OUT STD_LOGIC_VECTOR(0 TO 7));
END dec3to8;
ARCHITECTURE Behavior OF dec3to8 IS
BEGIN
PROCESS (W, En)
BEGIN
    IF En = '1' THEN
        CASE W IS
            WHEN "000" => Y <= "10000000";
            WHEN "001" => Y <= "01000000";
            WHEN "010" => Y <= "00100000";
            WHEN "011" => Y <= "00010000";
            WHEN "100" => Y <= "00001000";
            WHEN "101" => Y <= "00000100";
            WHEN "110" => Y <= "00000010";
            WHEN "111" => Y <= "00000001";
        END CASE;
    ELSE
        Y <= "00000000";
    END IF;
END PROCESS;
END Behavior;
```

5.10 TO 1 MULTIPLEXER:

```
LIBRARY ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
ENTITY minel0to1mux IS
PORT ( Din, R0, R1 , R2, R3, R4, R5, R6, R7, Gout : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
      sel : IN STD_LOGIC_VECTOR(0 TO 9);
      Outmux : OUT STD_LOGIC_VECTOR(8 DOWNTO 0));
```

```

END mine10to1mux;
architecture structural of mine10to1mux is

BEGIN
PROCESS (sel)
BEGIN
IF sel = "1000000000" THEN
    Outmux <= R0;
ELSIF sel = "0100000000" THEN
    Outmux <= R1;
ELSIF sel = "0010000000" THEN
    Outmux <= R2;
ELSIF sel = "0001000000" THEN
    Outmux <= R3;
ELSIF sel = "0000100000" THEN
    Outmux <= R4;
ELSIF sel = "0000010000" THEN
    Outmux <= R5;
ELSIF sel = "0000001000" THEN
    Outmux <= R6;
ELSIF sel = "0000000100" THEN
    Outmux <= R7;
ELSIF sel = "0000000010" THEN
    Outmux <= Gout;
ELSE
    Outmux <= Din;
END IF;
END PROCESS;
end structural;

```

6.PC:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;
USE ieee.std_logic_signed.all;

ENTITY PC IS
PORT (      D: IN STD_LOGIC_VECTOR(8 DOWNTO 0);
        CLK, Reset, E, L: IN STD_LOGIC;
        Q: OUT STD_LOGIC_VECTOR(8 downto 0));
END PC;
ARCHITECTURE Behavioral OF PC IS

BEGIN
PROCESS(CLK, Reset)
VARIABLE count: STD_LOGIC_VECTOR (8 downto 0);
BEGIN
IF (Reset = '0') THEN
    Count := (others => '0');
ELSIF rising_edge(CLK) THEN
    IF E = '1' THEN
        count := count + "000000001";
    ELSIF L = '1' THEN
        count := D;
    END IF;
    Q <= count;
END IF;
END PROCESS;
END Behavioral;

```

7. MEMORY:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity memory is
generic(
    addr_width : integer := 128;
    addr_bits  : integer := 7;
    data_width  : integer := 9
);
port( DATA_IN : in std_logic_vector(data_width-1 downto 0);
      ADDR     : in std_logic_vector(addr_bits-1 downto 0);
      Clk      : in std_logic;
      Write_EN : in std_logic;
      DATA_OUT : out std_logic_vector(data_width-1 downto 0)
);
end memory;

architecture arch of memory is
type ram_type is array (0 to addr_width-1) of std_logic_vector(data_width-1 downto 0);
signal user_RAM : ram_type;
attribute ram_init_file : string;
attribute ram_init_file of user_RAM : signal is "ram_data.mif";
begin
process(Clk, Write_EN)
begin
if Rising_edge(Clk) then
    if Write_EN = '1' then
        user_RAM(to_integer(unsigned(ADDR))) <= DATA_IN;
    end if;
end if;
end process;
DATA_OUT <= user_RAM (to_integer(unsigned(ADDR))) WHEN (Write_EN = '0')
ELSE "000000000";
end arch;
```

II) VHDL code for complex components:

1. FSM CONTROL UNIT:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;
USE ieee.std_logic_unsigned.all;
ENTITY FSM_controlunit IS
PORT (
    clk, Reset, Run: IN std_logic;
    I, G: IN std_logic_vector(8 DOWNTO 0);

    G_O, Din_O: OUT std_logic;
    R_O: OUT std_logic_vector(0 TO 7);

    IR_I, ADD_SUB, A_I, G_I: OUT std_logic;
    ADDR_I, DOUT_I: OUT std_logic;
    R_I : OUT STD_LOGIC_VECTOR(0 TO 7);
    Done, incr_PC, W_D: BUFFER std_logic);
END FSM_controlunit;
ARCHITECTURE behavior OF FSM_controlunit IS
COMPONENT dec3to8
PORT (
    W : IN STD_LOGIC_VECTOR(2 DOWNTO 0);
    En : IN STD_LOGIC;
    Y : OUT STD_LOGIC_VECTOR(0 TO 7));
END COMPONENT;
```

```

    TYPE state IS (IWAIT, INITIAL, MV, MVI1, MVI2, MVI3, ADD1, ADD2, ADD3, SUB1, SUB2,
SUB3, LD1, LD2, ST1, ST2, MVNZ);
    SIGNAL pr_state, nx_state: state;
    SIGNAL RX_TEMP, RY_TEMP, R7_TEMP: STD_LOGIC_VECTOR (0 TO 7);
    SIGNAL clear: STD_LOGIC;
BEGIN
clear <= reset or done;
cst_pr: PROCESS(clk, clear)
    BEGIN
        IF (clear = '0') THEN
            pr_state <= IWAIT;
        ELSIF (rising_edge(clk)) THEN
            pr_state <= nx_state;
        END IF;
    END PROCESS cst_pr;

nxt_pr: PROCESS (RUN, I(8 DOWNT0 6), pr_state, Done, G)
BEGIN
    CASE pr_state IS
        WHEN IWAIT =>
            IF RUN = '1' THEN
                nx_state <= IWAIT;
            ELSIF (RUN = '0') THEN
                nx_state <= INITIAL;
            END IF;

        WHEN INITIAL =>
            IF (I(8 DOWNT0 6) = "000") THEN
                nx_state <= MV;
            ELSIF (I(8 DOWNT0 6) = "001") THEN
                nx_state <= MVI1;
            ELSIF (I(8 DOWNT0 6) = "010") THEN
                nx_state <= ADD1;
            ELSIF (I(8 DOWNT0 6) = "011") THEN
                nx_state <= SUB1;
            ELSIF (I(8 DOWNT0 6) = "100") THEN
                nx_state <= LD1;
            ELSIF (I(8 DOWNT0 6) = "101") THEN
                nx_state <= ST1;
            ELSIF (I(8 DOWNT0 6) = "110") THEN
                nx_state <= MVNZ;
            END IF;

        WHEN MV =>
            IF (Done = '1') THEN
                nx_state <= IWAIT;
            ELSE
                nx_state <= MV;
            END IF;

        WHEN MVI1 =>
            nx_state <= MVI2;
        WHEN MVI2 =>
            nx_state <= MVI3;
        WHEN MVI3 =>
            IF (Done = '1') THEN
                nx_state <= IWAIT;
            ELSE
                nx_state <= MVI3;
            END IF;

        WHEN ADD1 =>
            nx_state <= ADD2;

```

```

    WHEN ADD2 =>
        nx_state <= ADD3;
    WHEN ADD3 =>
        IF (Done = '1') THEN
            nx_state <= IWAIT;
        ELSE
            nx_state <= ADD3;
        END IF;

    WHEN SUB1 =>
        nx_state <= SUB2;
    WHEN SUB2 =>
        nx_state <= SUB3;
    WHEN SUB3 =>
        IF (Done = '1') THEN
            nx_state <= IWAIT;
        ELSE
            nx_state <= SUB3;
        END IF;

    WHEN LD1 =>
        nx_state <= LD2;
    WHEN LD2 =>
        IF (Done = '1') THEN
            nx_state <= IWAIT;
        ELSE
            nx_state <= LD2;
        END IF;

    WHEN ST1 =>
        nx_state <= ST2;
    WHEN ST2 =>
        IF (Done = '1') THEN
            nx_state <= IWAIT;
        ELSE
            nx_state <= ST2;
        END IF;

    WHEN MVNZ =>
        IF (Done = '1') THEN
            nx_state <= IWAIT;
        ELSE
            nx_state <= MVNZ;
        END IF;

    WHEN OTHERS =>
        nx_state <= IWAIT;
    END CASE;
END PROCESS nxt_pr;

Idec3to8_X: dec3to8 PORT MAP ( I(5 DOWNT0 3), '1', RX_TEMP);
Idec3to8_Y: dec3to8 PORT MAP ( I(2 DOWNT0 0), '1', RY_TEMP);
Idec3to8_7: dec3to8 PORT MAP ( "111", '1', R7_TEMP);

out_pr: PROCESS(pr_state)
BEGIN
    CASE pr_state IS
        WHEN IWAIT =>
            IR_I <= '1';
            R_I <= "00000000";
            A_I <= '0';
            G_I <= '0';
            R_O <= R7_TEMP;
    
```

```

G_O <= '0';
Din_O <= '0';
DONE <= '0';
ADDR_I <= '1';
DOUT_I <= '0';
W_D <= '0';
incr_PC <= '0';

WHEN INITIAL =>
IR_I <= '0';
R_I <= "00000000";
A_I <= '0';
G_I <= '0';
R_O <= "00000000";
G_O <= '0';
Din_O <= '0';
DONE <= '0';
ADDR_I <= '0';
DOUT_I <= '0';
W_D <= '0';
incr_PC <= '0';

WHEN MV =>
IR_I <= '0';
R_I <= RX_TEMP;
A_I <= '0';
G_I <= '0';
R_O <= RY_TEMP;
G_O <= '0';
Din_O <= '0';
DONE <= '1';
ADDR_I <= '0';
DOUT_I <= '0';
W_D <= '0';
IF (RX_TEMP = "00000001") THEN
    incr_PC <= '0';
ELSE
    incr_PC <= '1';
END IF;

WHEN MVI1 =>
IR_I <= '0';
R_I <= "00000000";
A_I <= '0';
G_I <= '0';
R_O <= "00000000";
G_O <= '0';
Din_O <= '0';
DONE <= '0';
ADDR_I <= '0';
DOUT_I <= '0';
W_D <= '0';
incr_PC <= '1';
WHEN MVI2 =>
IR_I <= '0';
R_I <= "00000000";
A_I <= '0';
G_I <= '0';
R_O <= R7_TEMP;
G_O <= '0';
Din_O <= '0';
DONE <= '0';
ADDR_I <= '1';

```



```

        DOUT_I <= '0';
        W_D <= '0';
        incr_PC <= '0';
        WHEN MVI3 =>
            IR_I <= '0';
            R_I <= RX_TEMP;
A_I <= '0';
        G_I <= '0';
        R_O <= "00000000";
        G_O <= '0';
        Din_O <= '1';
        DONE <= '1';
        ADDR_I <= '0';
        DOUT_I <= '0';
        W_D <= '0';
        IF (RX_TEMP = "00000001") THEN
            incr_PC <= '0';
        ELSE
            incr_PC <= '1';
END IF;

        WHEN ADD1 =>
            IR_I <= '0';
R_I <= "00000000";
        A_I <= '1';
        G_I <= '0';
        R_O <= RX_TEMP;
        G_O <= '0';
        Din_O <= '0';
        DONE <= '0';
ADDR_I <= '0';
        DOUT_I <= '0';
        W_D <= '0';
incr_PC <= '0';
        WHEN ADD2 =>
            IR_I <= '0';
R_I <= "00000000";
        A_I <= '0';
        G_I <= '1';
        R_O <= RY_TEMP;
        Din_O <= '0';
        G_O <= '0';
        DONE <= '0';
        ADD_SUB <= '0';
        ADDR_I <= '0';
        DOUT_I <= '0';
        W_D <= '0';
incr_PC <= '0';
        WHEN ADD3 =>
            IR_I <= '0';
R_I <= RX_TEMP;
        A_I <= '0';
        G_I <= '0';
        R_O <= "00000000";
        Din_O <= '0';
        G_O <= '1';
        DONE <= '1';
        ADDR_I <= '0';
        DOUT_I <= '0';
        W_D <= '0';
        IF (RX_TEMP = "00000001") THEN
            incr_PC <= '0';
        ELSE

```

```

        incr_PC <= '1';
END IF;

    WHEN SUB1 =>
        IR_I <= '0';
        R_I <= "00000000";
        A_I <= '1';
        G_I <= '0';
        R_O <= RX_TEMP;
        G_O <= '0';
        Din_O <= '0';
        DONE <= '0';
        ADDR_I <= '0';
        DOUT_I <= '0';
        W_D <= '0';
incr_PC <= '0';
    WHEN SUB2 =>
        IR_I <= '0';
        R_I <= "00000000";
        A_I <= '0';
        G_I <= '1';
        R_O <= RY_TEMP;
        Din_O <= '0';
        G_O <= '0';
        DONE <= '0';
        ADDR_I <= '0';
        DOUT_I <= '0';
        W_D <= '0';
incr_PC <= '0';
        ADD_SUB <= '1';
    WHEN SUB3 =>
        IR_I <= '0';
        R_I <= RX_TEMP;
        A_I <= '0';
        G_I <= '0';
        R_O <= "00000000";
        Din_O <= '0';
        G_O <= '1';
        DONE <= '1';
        ADDR_I <= '0';
        DOUT_I <= '0';
        W_D <= '0';
        IF (RX_TEMP = "00000001") THEN
            incr_PC <= '0';
        ELSE
            incr_PC <= '1';
END IF;

    WHEN LD1 =>
        IR_I <= '0';
        R_I <= "00000000";
        A_I <= '0';
        G_I <= '0';
        R_O <= RY_TEMP;
        Din_O <= '0';
        G_O <= '0';
        DONE <= '0';
        ADDR_I <= '1';
        DOUT_I <= '0';
        W_D <= '0';
incr_PC <= '0';
    WHEN LD2 =>
        IR_I <= '0';

```

```

R_I <= RX_TEMP;
A_I <= '0';
G_I <= '0';
R_O <= "000000000";
Din_O <= '1';
G_O <= '0';
DONE <= '1';
ADDR_I <= '0';
DOUT_I <= '0';
W_D <= '0';
IF (RX_TEMP = "000000001") THEN
    incr_PC <= '0';
ELSE
    incr_PC <= '1';
END IF;

```

```

WHEN ST1 =>
    IR_I <= '0';
    R_I <= "000000000";
    A_I <= '0';
    G_I <= '0';
    R_O <= RX_TEMP;
    Din_O <= '0';
    G_O <= '0';
    DONE <= '0';
    ADDR_I <= '0';
    DOUT_I <= '1';
    W_D <= '0';
    incr_PC <= '0';
WHEN ST2 =>
    IR_I <= '0';
    R_I <= "000000000";
    A_I <= '1';
    G_I <= '0';
    R_O <= RY_TEMP;
    Din_O <= '0';
    G_O <= '0';
    DONE <= '1';
    ADDR_I <= '1';
    DOUT_I <= '0';
    W_D <= '1';
    incr_PC <= '1';

```

```

WHEN MVNZ =>
    IF (G = "000000000") THEN
        IR_I <= '0';
        R_I <= "000000000";
        A_I <= '0';
        G_I <= '0';
        R_O <= "000000000";
        G_O <= '0';
        Din_O <= '0';
        DONE <= '1';
        ADDR_I <= '0';
        DOUT_I <= '0';
        W_D <= '0';
        incr_PC <= '1';
    ELSE

```

```

        IR_I <= '0';
        R_I <= RX_TEMP;
        A_I <= '0';
        G_I <= '0';
        R_O <= RY_TEMP;

```

```

        G_O <= '0';
        Din_O <= '0';
        DONE <= '1';
        ADDR_I <= '0';
        DOUT_I <= '0';
        W_D <= '0';
        IF (RX_TEMP = "00000001") THEN
            incr_PC <= '0';
        ELSE
            incr_PC <= '1';
        END IF;
    END IF;

    WHEN OTHERS =>
        DONE <= '0';
    END CASE;
END PROCESS out_pr;
END behavior;

```

2. PROCESSOR:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;
USE ieee.std_logic_signed.all;
USE ieee.numeric_std.all;
ENTITY Processor IS
PORT (
    clk, Reset, Run: IN std_logic;
    DIN : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
    HEX4, HEX5: OUT STD_LOGIC_VECTOR(0 TO 6);
    Done: BUFFER STD_LOGIC;
    W: BUFFER STD_LOGIC;
    ADDR, DOUT: BUFFER STD_LOGIC_VECTOR(8 DOWNTO 0)
);
END Processor;
ARCHITECTURE Behavior OF Processor IS
COMPONENT FSM_controlunit
PORT (
    clk, Reset, Run: IN std_logic;
    I, G: IN std_logic_vector(8 DOWNTO 0);

    G_O, Din_O: OUT std_logic;
    R_O: OUT std_logic_vector(0 TO 7);

    IR_I, ADD_SUB, A_I, G_I: OUT std_logic;
    ADDR_I, DOUT_I: OUT std_logic;
    R_I : OUT STD_LOGIC_VECTOR(0 TO 7);
    Done, incr_PC, W_D: BUFFER std_logic);
END COMPONENT;

COMPONENT regn
generic (n: natural:= 9);
PORT (
    D : IN STD_LOGIC_VECTOR(n-1 downto 0);
    Clk, Reset, Load :IN STD_LOGIC;
    Q : OUT STD_LOGIC_VECTOR(n-1 downto 0));
END COMPONENT;

COMPONENT PC IS
PORT (
    D: IN STD_LOGIC_VECTOR(8 DOWNTO 0);
    CLK, RESET, E, L: IN STD_LOGIC;
    Q: OUT STD_LOGIC_VECTOR(8 downto 0));
END COMPONENT;

COMPONENT mineDFFpositive_edge IS

```

```

PORT (D, Clk, RESET : IN STD_LOGIC;
      Q : OUT STD_LOGIC);
END COMPONENT;

COMPONENT mine10to1mux
PORT ( Din, R0, R1 , R2, R3, R4, R5, R6, R7, Gout : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
      sel : IN STD_LOGIC_VECTOR(0 TO 9);
      Outmux : OUT STD_LOGIC_VECTOR(8 DOWNTO 0));
END COMPONENT;

COMPONENT my_7seghex IS
PORT (      C: IN STD_LOGIC_VECTOR(3 DOWNTO 0);
      Z : OUT STD_LOGIC_VECTOR(0 TO 6));
END COMPONENT;

SIGNAL R_O, R_I: STD_LOGIC_VECTOR(0 TO 7);
SIGNAL G_O, Din_O, IR_I, ADD_SUB, A_I, G_I, E, L, ADDR_I, DOUT_I, W_D, incr_PC: STD_LOGIC;
SIGNAL R_OUT_0, R_OUT_1, R_OUT_2, R_OUT_3, R_OUT_4, R_OUT_5, R_OUT_6, PC_OUT :
STD_LOGIC_VECTOR(8 DOWNTO 0);
SIGNAL A_OUT, ADD_SUB_RES, G_OUT, DIN_IR, BusWires: STD_LOGIC_VECTOR(8 DOWNTO 0);
SIGNAL COUT : STD_LOGIC;
SIGNAL Sel : STD_LOGIC_VECTOR(0 to 9);
--SIGNAL ADDR, DOUT: STD_LOGIC_VECTOR(8 DOWNTO 0);
BEGIN

iFSM_controlunit: FSM_controlunit PORT MAP(clk => clk,
Reset => Reset,
Run => Run,
I(8 DOWNTO 0) => DIN_IR(8 DOWNTO 0),
G(8 DOWNTO 0) => G_OUT(8 DOWNTO 0),
G_O => G_O,
Din_O => Din_O,
R_O(0 TO 7) => R_O(0 TO 7),
IR_I => IR_I,
ADD_SUB => ADD_SUB,
A_I => A_I,
G_I => G_I,
ADDR_I => ADDR_I,
DOUT_I => DOUT_I,
R_I(0 TO 7) => R_I(0 TO 7),
Done => Done,
incr_PC => incr_PC,
W_D => W_D);

iregn_0: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, R_I(0), R_OUT_0(8 DOWNTO 0));
iregn_1: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, R_I(1), R_OUT_1(8 DOWNTO 0));
iregn_2: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, R_I(2), R_OUT_2(8 DOWNTO 0));
iregn_3: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, R_I(3), R_OUT_3(8 DOWNTO 0));
iregn_4: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, R_I(4), R_OUT_4(8 DOWNTO 0));
iregn_5: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, R_I(5), R_OUT_5(8 DOWNTO 0));
iregn_6: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, R_I(6), R_OUT_6(8 DOWNTO 0));
iPC: PC PORT MAP(BusWires(8 DOWNTO 0), Clk, RESET, incr_PC, R_I(7), PC_OUT(8 DOWNTO 0));
iregn_A: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, A_I, A_OUT(8 DOWNTO 0));
iregn_G: regn PORT MAP(ADD_SUB_RES(8 DOWNTO 0), Clk, Reset, G_I, G_OUT(8 DOWNTO 0));
iregn_IR: regn PORT MAP(DIN(8 DOWNTO 0), Clk, Reset, IR_I, DIN_IR(8 DOWNTO 0));
iregn_ADDR: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, ADDR_I, ADDR(8 DOWNTO 0));
iregn_DOUT: regn PORT MAP(BusWires(8 DOWNTO 0), Clk, Reset, DOUT_I, DOUT(8 DOWNTO 0));
iregn_WD: mineDFFpositive_edge PORT MAP(W_D, clk, Reset,W);

Sel <= R_O & G_O & Din_O;
Imine10to1mux: mine10to1mux PORT MAP(DIN(8 DOWNTO 0) => DIN(8 DOWNTO 0),
R0(8 DOWNTO 0) => R_OUT_0(8 DOWNTO 0),
R1(8 DOWNTO 0) => R_OUT_1(8 DOWNTO 0),

```

```

R2(8 DOWNT0 0) => R_OUT_2(8 DOWNT0 0),
R3(8 DOWNT0 0) => R_OUT_3(8 DOWNT0 0),
R4(8 DOWNT0 0) => R_OUT_4(8 DOWNT0 0),
R5(8 DOWNT0 0) => R_OUT_5(8 DOWNT0 0),
R6(8 DOWNT0 0) => R_OUT_6(8 DOWNT0 0),
R7(8 DOWNT0 0) => PC_OUT(8 DOWNT0 0),
Gout(8 DOWNT0 0) => G_OUT(8 DOWNT0 0),
sel(0 TO 9) => sel (0 TO 9),
Outmux(8 DOWNT0 0) => BusWires(8 DOWNT0 0));

alu: PROCESS (ADD_SUB, A_OUT, BusWires)
BEGIN
    IF ADD_SUB = '0' THEN
        ADD_SUB_RES <= A_OUT + BusWires;
    ELSE
        ADD_SUB_RES <= A_OUT - BusWires;
    END IF;
END PROCESS;

imy_7seghex_4: my_7seghex PORT MAP (R_OUT_4(3 DOWNT0 0), HEX4(0 TO 6));
imy_7seghex_5: my_7seghex PORT MAP (R_OUT_5(3 DOWNT0 0), HEX5(0 TO 6));
END Behavior;

```

3.OVERALL CODE FOR LAB 6:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;
USE ieee.std_logic_signed.all;
USE ieee.numeric_std.all;
ENTITY lab6 IS
PORT (
    clk, Reset, Run: IN std_logic;
    Done: BUFFER STD_LOGIC;
    HEX0, HEX1, HEX2, HEX3, HEX4, HEX5: OUT STD_LOGIC_VECTOR(0 TO 6);
    LEDs: OUT STD_LOGIC_VECTOR(8 DOWNT0 0));
END lab6;
ARCHITECTURE Behavior OF lab6 IS

COMPONENT Processor
PORT (
    clk, Reset, Run: IN std_logic;
    DIN : IN STD_LOGIC_VECTOR(8 DOWNT0 0);
    HEX4, HEX5: OUT STD_LOGIC_VECTOR(0 TO 6);
    Done: BUFFER STD_LOGIC;
    W: BUFFER STD_LOGIC;
    ADDR, DOUT: BUFFER STD_LOGIC_VECTOR(8 DOWNT0 0)
);
END COMPONENT;

COMPONENT memory
generic(
    addr_width : integer := 128;
    addr_bits : integer := 7;
    data_width : integer := 9
);
port( DATA_IN : in std_logic_vector(data_width-1 downto 0);
    ADDR : in std_logic_vector(addr_bits-1 downto 0);
    Clk : in std_logic;
    Write_EN : in std_logic;
    DATA_OUT : out std_logic_vector(data_width-1 downto 0)
);
end COMPONENT;

```

```

COMPONENT regn
generic (n: natural:= 9);
PORT (      D : IN STD_LOGIC_VECTOR(n-1 downto 0);
        Clk, Reset, Load :IN STD_LOGIC;
        Q : OUT STD_LOGIC_VECTOR(n-1 downto 0));
END COMPONENT;

COMPONENT my_7seghex IS
PORT (      C: IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        Z : OUT STD_LOGIC_VECTOR(0 TO 6));
END COMPONENT;

SIGNAL WR_en, ADDR7xnoR8, ADDRn7xnoR8, W, WRen, E: STD_LOGIC;
SIGNAL ADDR, DOUT, Din, DATA_OUT, DATA_IN: STD_LOGIC_VECTOR(8 DOWNTO 0);
SIGNAL ADDR_mem: STD_LOGIC_VECTOR(6 DOWNTO 0);
BEGIN
DATA_IN <= DOUT;
Din <= DATA_OUT;
ADDR_mem <= ADDR(6 DOWNTO 0);

ADDR7xnoR8 <= ADDR(7) xnor ADDR(8);
ADDRn7xnoR8 <= NOT(ADDR(7)) xnor ADDR(8);
WR_en <= W AND ADDR7xnoR8;
E <= W AND ADDRn7xnoR8;

iProcessor: Processor PORT MAP(clk, Reset, Run, Din, HEX4, HEX5, Done, W, ADDR, DOUT);
imemory: memory PORT MAP(DATA_IN, ADDR_mem, Clk, WR_en, DATA_OUT);
iregn: regn PORT MAP(DOUT, Clk, reset, E, LEDs);
imy_7seghex_0: my_7seghex PORT MAP (Din(3 DOWNTO 0), HEX0(0 TO 6));
imy_7seghex_1: my_7seghex PORT MAP (Din(7 DOWNTO 4), HEX1(0 TO 6));
imy_7seghex_2: my_7seghex PORT MAP ("000" & Din(8), HEX2(0 TO 6));
imy_7seghex_3: my_7seghex PORT MAP (ADDR(3 DOWNTO 0), HEX3(0 TO 6));
END Behavior;

```

III) VHDL code for testing instructions:

1. TESTING MVI - MVNZ - ADD - SUB:

```

WIDTH=9;
DEPTH=128;

ADDRESS_RADIX=UNS;
DATA_RADIX=BIN;

CONTENT BEGIN
    0      :    001100000;
    1      :    000000011;
    2      :    110101100;
    3      :    000101100;
    4      :    010100101;
    5      :    110101100;
    6      :    011100101;
    [7..127] :    000000000;
END;

```

2.TEST LOAD INSTRUCTION:

```
WIDTH=9;
DEPTH=128;

ADDRESS_RADIX=UNS;
DATA_RADIX=BIN;

CONTENT BEGIN
    0      :    001100000;
    1      :    000000011;
    2      :    001101000;
    3      :    000001010;
    4      :    100100101;
    [5..9] :    000000000;
    10     :    000001111;
    [11..127] :    000000000;
END;
```

3.TEST STORE INSTRUCTION:

```
WIDTH=9;
DEPTH=128;

ADDRESS_RADIX=UNS;
DATA_RADIX=BIN;

CONTENT BEGIN
    0      :    001100000;
    1      :    000000011;
    2      :    001101000;
    3      :    000000101;
    4      :    101100101;
    [5..127] :    000000000;
END;
```

4.TEST THE LEDS:

```
WIDTH=9;
DEPTH=128;

ADDRESS_RADIX=UNS;
DATA_RADIX=BIN;

CONTENT BEGIN
    0      :    001100000;
    1      :    000000011;
    2      :    001101000;
    3      :    010000101;
    4      :    101100101;
    [5..127] :    000000000;
END;
```


5. TEST MVI MV OF R7:

```
WIDTH=9;
DEPTH=128;

ADDRESS_RADIX=UNS;
DATA_RADIX=BIN;

CONTENT BEGIN
    0      :    001100000;
    1      :    000001010;
    2      :    000111100;
    [3..9] :    000000000;
    10     :    001111000;
    11     :    000001111;
    [12..14] :    000000000;
    15     :    000001000;
    [16..127] :    000000000;
END;
```

6. TEST MVNZ, ADD, SUB OF R7:

```
WIDTH=9;
DEPTH=128;

ADDRESS_RADIX=UNS;
DATA_RADIX=BIN;

CONTENT BEGIN
    0      :    001100000;
    1      :    000001010;
    2      :    110111100;
    3      :    010100000;
    4      :    110111100;
    [5..6] :    000000000;
    7      :    000001000;
    [8..9] :    000000000;
    10     :    001101000;
    11     :    000000101;
    12     :    011111101;
    [13..127] :    000000000;
END;
```

7. TEST LOAD INSTRUCTIONS OF R7:

```
WIDTH=9;
DEPTH=128;

ADDRESS_RADIX=UNS;
DATA_RADIX=BIN;

CONTENT BEGIN
    0      :    001100000;
    1      :    000001010;
    2      :    100111100;
    [3..9] :    000000000;
    10     :    000001111;
    [11..14] :    000000000;
    15     :    000001000;
    [16..127] :    000000000;
END;
```

8. TEST LOOP:

```
WIDTH=9;
DEPTH=128;

ADDRESS_RADIX=UNS;
DATA_RADIX=BIN;

CONTENT BEGIN
    0      :    001010000;
    1      :    000000001;
    2      :    001100000;
    3      :    000000011;
    4      :    000101111;
    5      :    011100010;
    6      :    110111101;
    [7..127] :    000000000;
END;
```

9. STATE OUTPUT CODE:

```
WHEN IWAIT =>
    IR_I <= '1';
    R_I <= "00000000";
    A_I <= '0';
    G_I <= '0';
    R_O <= R7_TEMP;
    G_O <= '0';
    Din_O <= '0';
    DONE <= '0';
    ADDR_I <= '1';
    DOUT_I <= '0';
    W_D <= '0';
```

```

incr_PC <= '0';

WHEN INITIAL =>
IR_I <= '0';
R_I <= "00000000";
A_I <= '0';
G_I <= '0';
R_O <= "00000000";
G_O <= '0';
Din_O <= '0';
DONE <= '0';
ADDR_I <= '0';
DOUT_I <= '0';
W_D <= '0';
incr_PC <= '0';

WHEN MV =>
IR_I <= '0';
R_I <= RX_TEMP;
A_I <= '0';
G_I <= '0';
R_O <= RY_TEMP;
G_O <= '0';
Din_O <= '0';
DONE <= '1';
ADDR_I <= '0';
DOUT_I <= '0';
W_D <= '0';
IF (RX_TEMP = "00000001") THEN
    incr_PC <= '0';
ELSE
    incr_PC <= '1';
END IF;

```

```

WHEN MVI1 =>
IR_I <= '0';
R_I <= "00000000";
A_I <= '0';
G_I <= '0';
R_O <= "00000000";
G_O <= '0';
Din_O <= '0';
DONE <= '0';
ADDR_I <= '0';
DOUT_I <= '0';
W_D <= '0';
incr_PC <= '1';
WHEN MVI2 =>
IR_I <= '0';
R_I <= "00000000";
A_I <= '0';
G_I <= '0';

```

```

R_O <= R7_TEMP;
G_O <= '0';
Din_O <= '0';
DONE <= '0';
ADDR_I <= '1';
DOUT_I <= '0';
W_D <= '0';
incr_PC <= '0';
WHEN MVI3 =>
  IR_I <= '0';
  R_I <= RX_TEMP;
  A_I <= '0';
  G_I <= '0';
  R_O <= "00000000";
  G_O <= '0';
  Din_O <= '1';
  DONE <= '1';
  ADDR_I <= '0';
  DOUT_I <= '0';
  W_D <= '0';
  IF (RX_TEMP = "00000001") THEN
    incr_PC <= '0';
  ELSE
    incr_PC <= '1';
END IF;

```

```

  WHEN ADD1 =>
    IR_I <= '0';
  R_I <= "00000000";
  A_I <= '1';
  G_I <= '0';
  R_O <= RX_TEMP;
  G_O <= '0';
  Din_O <= '0';
  DONE <= '0';
  ADDR_I <= '0';
  DOUT_I <= '0';
  W_D <= '0';
  incr_PC <= '0';
  WHEN ADD2 =>
    IR_I <= '0';
    R_I <= "00000000";
    A_I <= '0';
    G_I <= '1';
    R_O <= RY_TEMP;
    Din_O <= '0';
    G_O <= '0';
    DONE <= '0';
    ADD_SUB <= '0';
    ADDR_I <= '0';
    DOUT_I <= '0';
    W_D <= '0';

```

```

incr_PC <= '0';
  WHEN ADD3 =>
    IR_I <= '0';
    R_I <= RX_TEMP;
    A_I <= '0';
    G_I <= '0';
    R_O <= "000000000";
    Din_O <= '0';
    G_O <= '1';
    DONE <= '1';
    ADDR_I <= '0';
    DOUT_I <= '0';
    W_D <= '0';
    IF (RX_TEMP = "000000001") THEN
      incr_PC <= '0';
    ELSE
      incr_PC <= '1';
    END IF;

```

```

  WHEN SUB1 =>
    IR_I <= '0';
    R_I <= "000000000";
    A_I <= '1';
    G_I <= '0';
    R_O <= RX_TEMP;
    G_O <= '0';
    Din_O <= '0';
    DONE <= '0';
    ADDR_I <= '0';
    DOUT_I <= '0';
    W_D <= '0';
    incr_PC <= '0';
  WHEN SUB2 =>
    IR_I <= '0';
    R_I <= "000000000";
    A_I <= '0';
    G_I <= '1';
    R_O <= RY_TEMP;
    Din_O <= '0';
    G_O <= '0';
    DONE <= '0';
    ADDR_I <= '0';
    DOUT_I <= '0';
    W_D <= '0';
    incr_PC <= '0';
    ADD_SUB <= '1';
  WHEN SUB3 =>
    IR_I <= '0';
    R_I <= RX_TEMP;
    A_I <= '0';
    G_I <= '0';
    R_O <= "000000000";

```

```

Din_O <= '0';
G_O <= '1';
DONE <= '1';
ADDR_I <= '0';
DOUT_I <= '0';
W_D <= '0';
IF (RX_TEMP = "00000001") THEN
    incr_PC <= '0';
ELSE
    incr_PC <= '1';
END IF;

```

```

WHEN LD1 =>
    IR_I <= '0';
    R_I <= "00000000";
    A_I <= '0';
    G_I <= '0';
    R_O <= RX_TEMP;
    Din_O <= '0';
    G_O <= '0';
    DONE <= '0';
    ADDR_I <= '1';
    DOUT_I <= '0';
    W_D <= '0';
    incr_PC <= '0';
WHEN LD2 =>
    IR_I <= '0';
    R_I <= RX_TEMP;
    A_I <= '0';
    G_I <= '0';
    R_O <= "00000000";
    Din_O <= '1';
    G_O <= '0';
    DONE <= '1';
    ADDR_I <= '0';
    DOUT_I <= '0';
    W_D <= '0';
    IF (RX_TEMP = "00000001") THEN
        incr_PC <= '0';
    ELSE
        incr_PC <= '1';
    END IF;

```

```

WHEN ST1 =>
    IR_I <= '0';
    R_I <= "00000000";
    A_I <= '0';
    G_I <= '0';
    R_O <= RX_TEMP;
    Din_O <= '0';
    G_O <= '0';
    DONE <= '0';

```

```

ADDR_I <= '0';
DOUT_I <= '1';
W_D <= '0';
incr_PC <= '0';
WHEN ST2 =>
  IR_I <= '0';
  R_I <= "00000000";
  A_I <= '1';
  G_I <= '0';
  R_O <= RY_TEMP;
  Din_O <= '0';
  G_O <= '0';
  DONE <= '1';
  ADDR_I <= '1';
  DOUT_I <= '0';
  W_D <= '1';
  incr_PC <= '1';


WHEN MVNZ =>
  IF (G = "00000000") THEN
    IR_I <= '0';
    R_I <= "00000000";
    A_I <= '0';
    G_I <= '0';
    R_O <= "00000000";
    G_O <= '0';
    Din_O <= '0';
    DONE <= '1';
    ADDR_I <= '0';
    DOUT_I <= '0';
    W_D <= '0';
    incr_PC <= '1';
  ELSE
    IR_I <= '0';
    R_I <= RX_TEMP;
    A_I <= '0';
    G_I <= '0';
    R_O <= RY_TEMP;
    G_O <= '0';
    Din_O <= '0';
    DONE <= '1';
    ADDR_I <= '0';
    DOUT_I <= '0';
    W_D <= '0';
    IF (RX_TEMP = "00000001") THEN
      incr_PC <= '0';
    ELSE
      incr_PC <= '1';
    END IF;
  END IF;
END IF;

```


B/WAVEFORM OBTAINED FROM EXPERIMENT AND STATE DIAGRAM:

D)Waveform of each code state when running:

 
1.Waveform obtained when running the code to check MV,MVI of R7:



 
2.Waveform obtained when running the code to check add,sub, and MVNZ of R7:



 
3.Waveform obtained when running the code to check LOAD of R7:



 
4. Waveform obtained when running the code to check mvi,mvz,mv,add,sub:



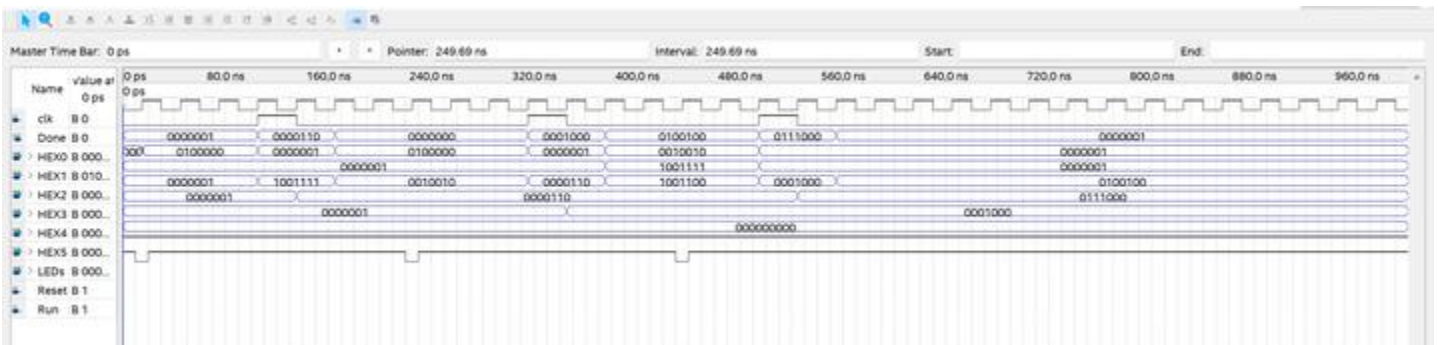
5. Waveform obtained when running the code to check LOAD instruction:



 
6. Waveform obtained when running the code to check STORE instruction:



 7. Waveform obtained when running the code to check the LEDs:





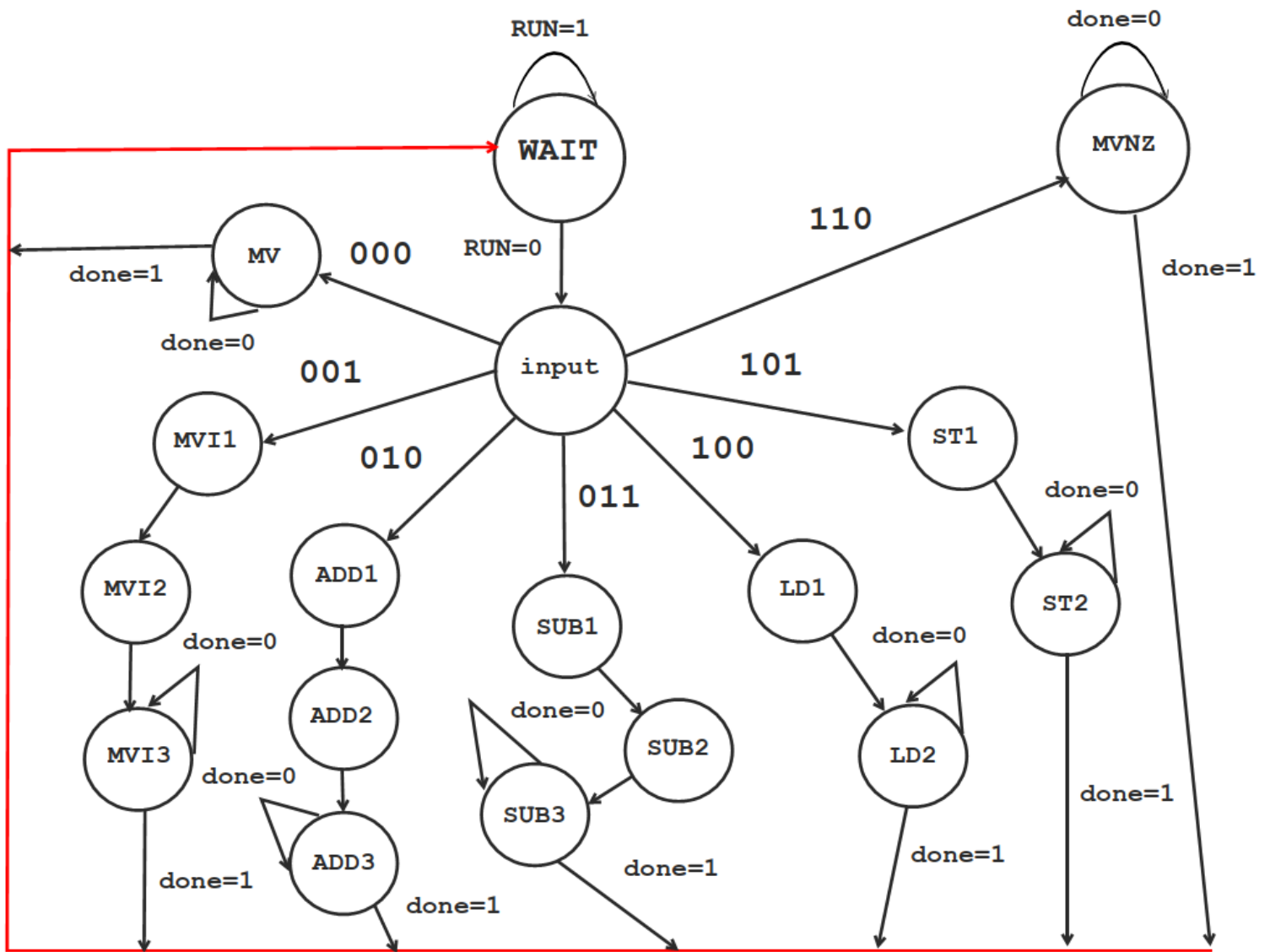II) State diagram of the FSM Control Unit:



C/RTL view – digital circuit obtained:

1.Register:

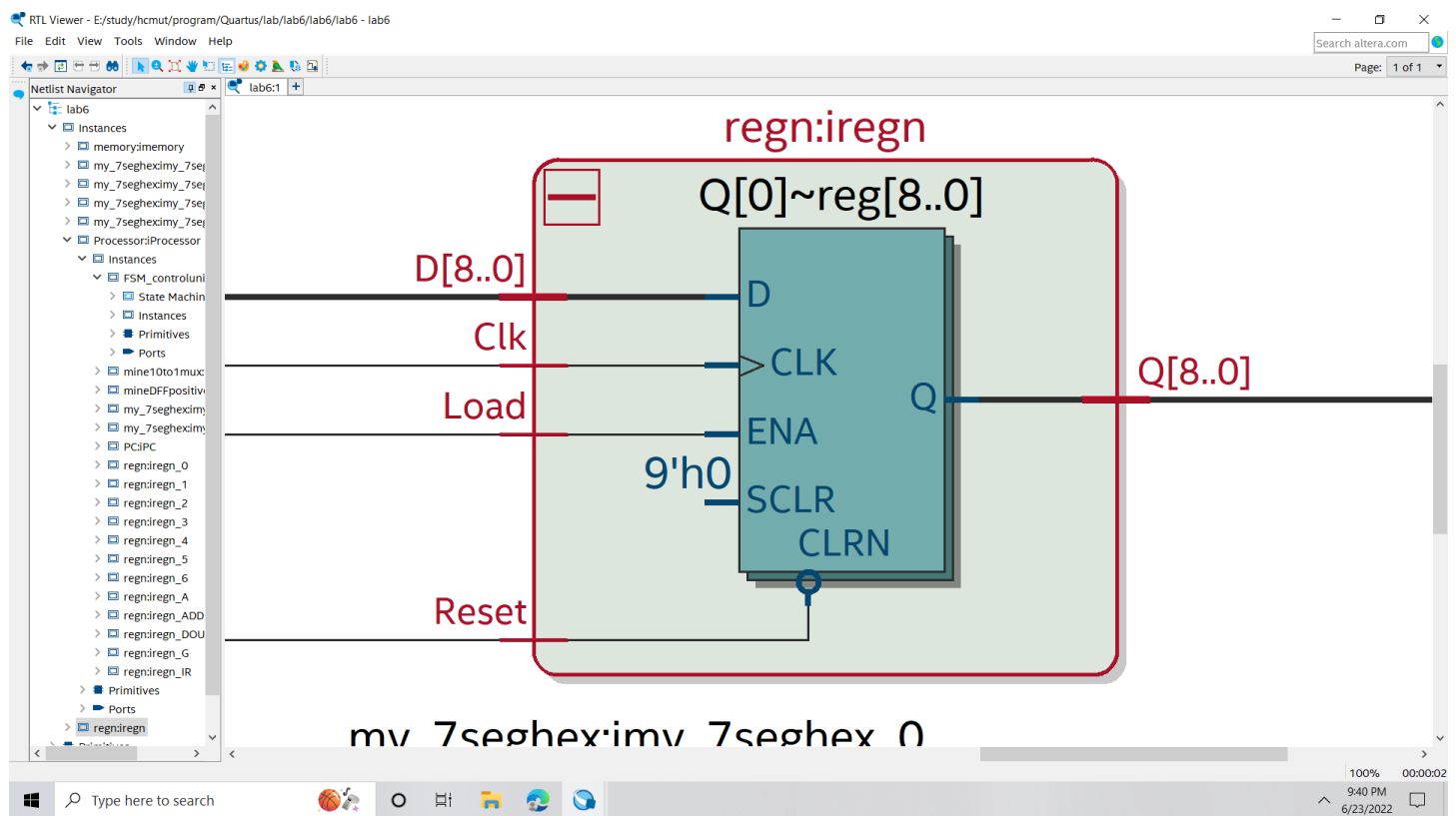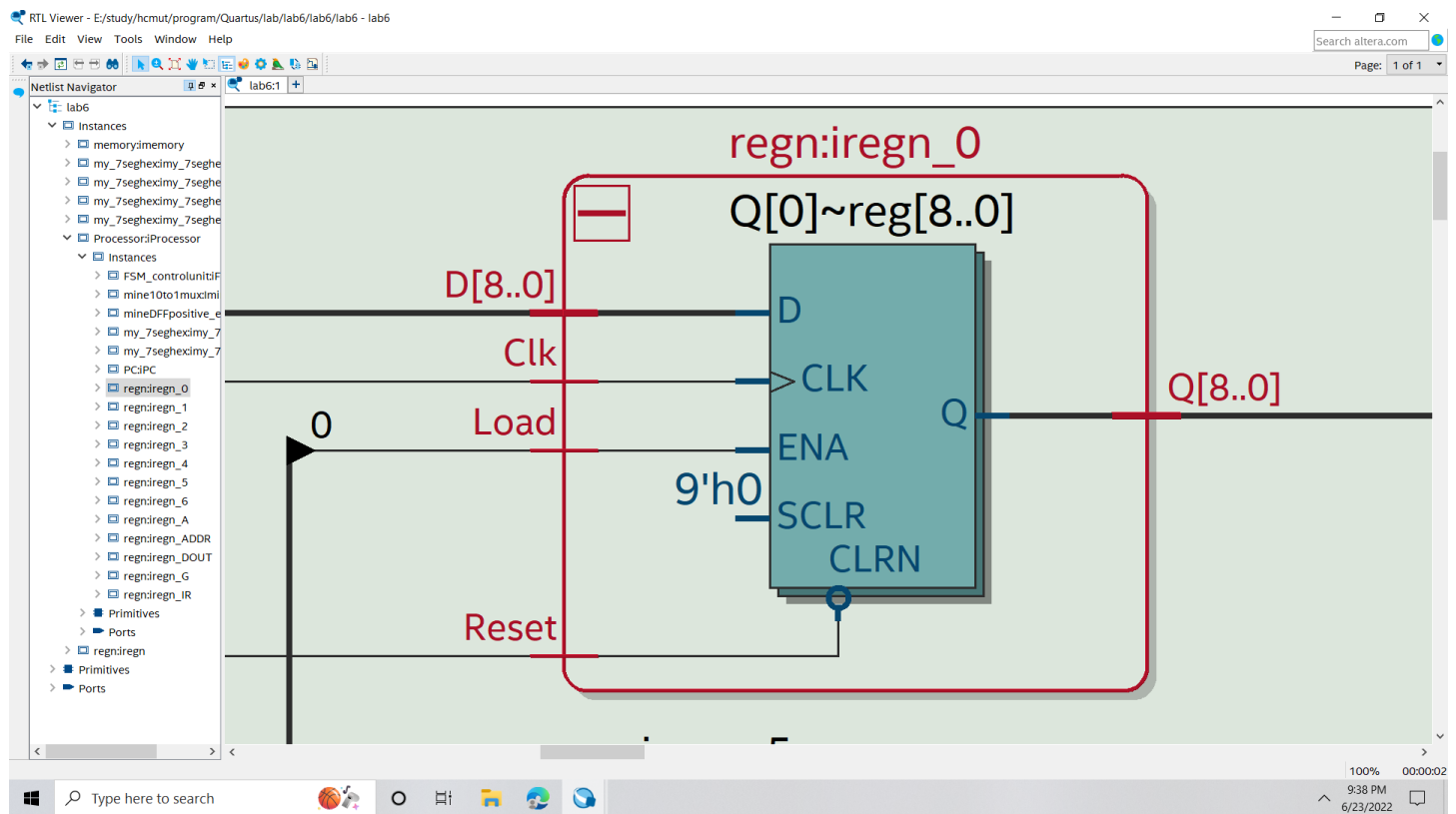

The screenshot displays the RTL Viewer interface for a Verilog HDL design. The design is titled "lab6" and is located in the project directory "E:/study/hcmut/program/Quartus/lab6/lab6/lab6 - lab6". The design is a 7-segment display driver, featuring a memory block, a processor block, and a 7-segment display block. The 7-segment display is composed of seven multiplexers (Mux0 to Mux6) that take data from the processor and output to the display segments. The design is named "my_7segheximny_7seghex_3".


The design includes the following components and connections:

- memory:imemory**: A memory block with inputs `Clk`, `IN[8.0]`, `DR[6.0]`, and `Write_EN`. It has an output `DATA_OUT[8.0]`.
- Processor:iProcessor**: A processor block with an input `ADDR[8.0]`.
- my_7segheximny_7seghex_3**: A 7-segment display block containing seven multiplexers (Mux0 to Mux6). Each multiplexer has a select input `SEL[3.0]` and a data input `DATA[15.0]`. The outputs of the multiplexers are connected to the 7-segment display segments: `HEX3[0.6]`, `Done`, `HEX4[0.6]`, `HEX5[0.6]`, `LEDs[8.0]`, `HEX0[0.6]`, `HEX1[0.6]`, and `HEX2[0.6]`.


The design is shown in the RTL Viewer, which displays the hierarchical structure of the design and the connections between the components. The design is named "my_7segheximny_7seghex_3".

The image shows a screenshot of the RTL Viewer application, displaying a Verilog HDL design for a D flip-flop. The design is titled "mineDFFpositive_edge:iregn_WD". The flip-flop is represented by a blue block with inputs D, CLK, SCLR, and CLRN, and output Q. The output Q is connected to a red line labeled "Q~reg0". The design is shown in the context of a Netlist Navigator on the left, which lists various components like memory, processors, and registers. The top of the window shows the RTL Viewer title bar and menu bar.


4) Decoder 3to8:

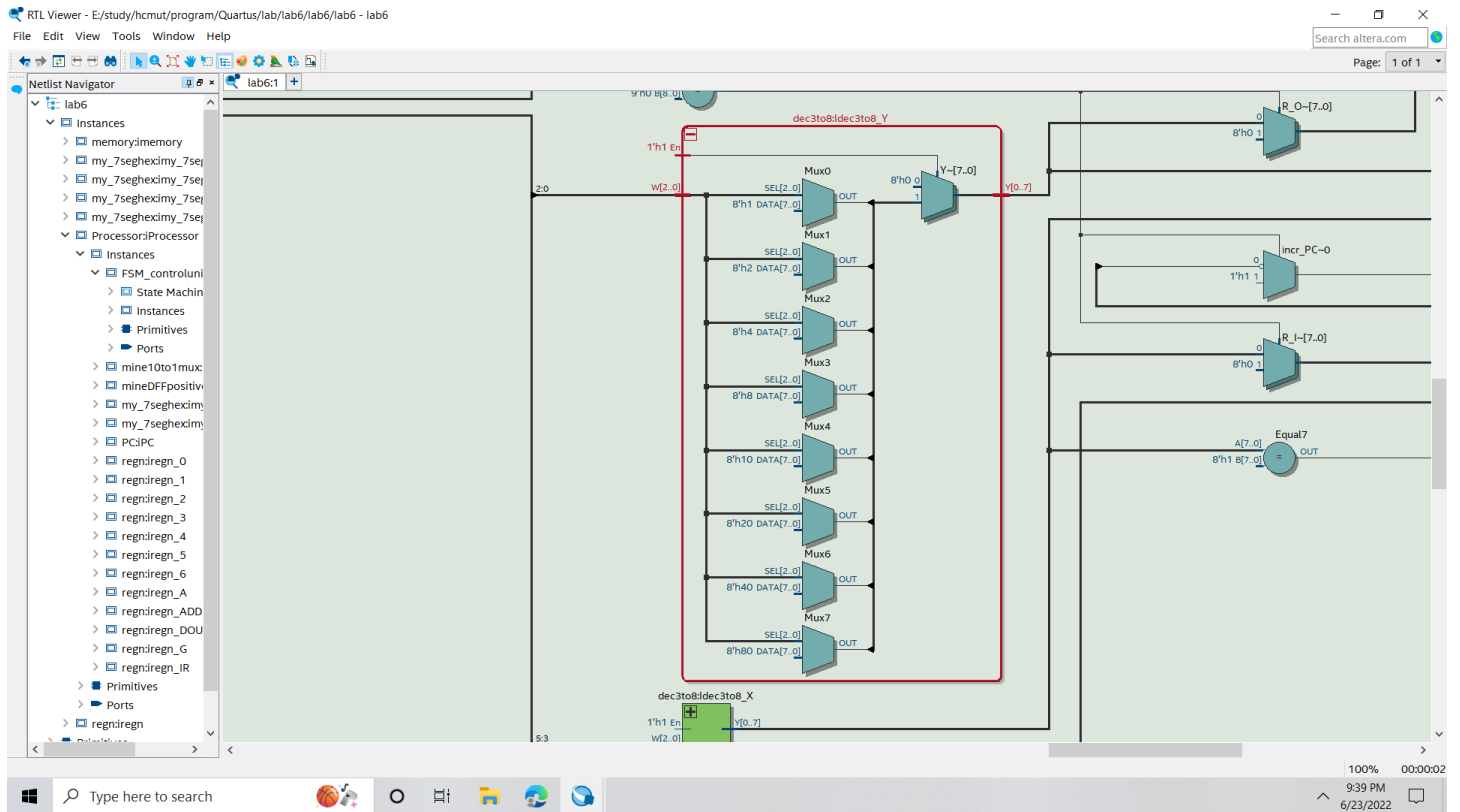


5) 10to1 multiplexer:

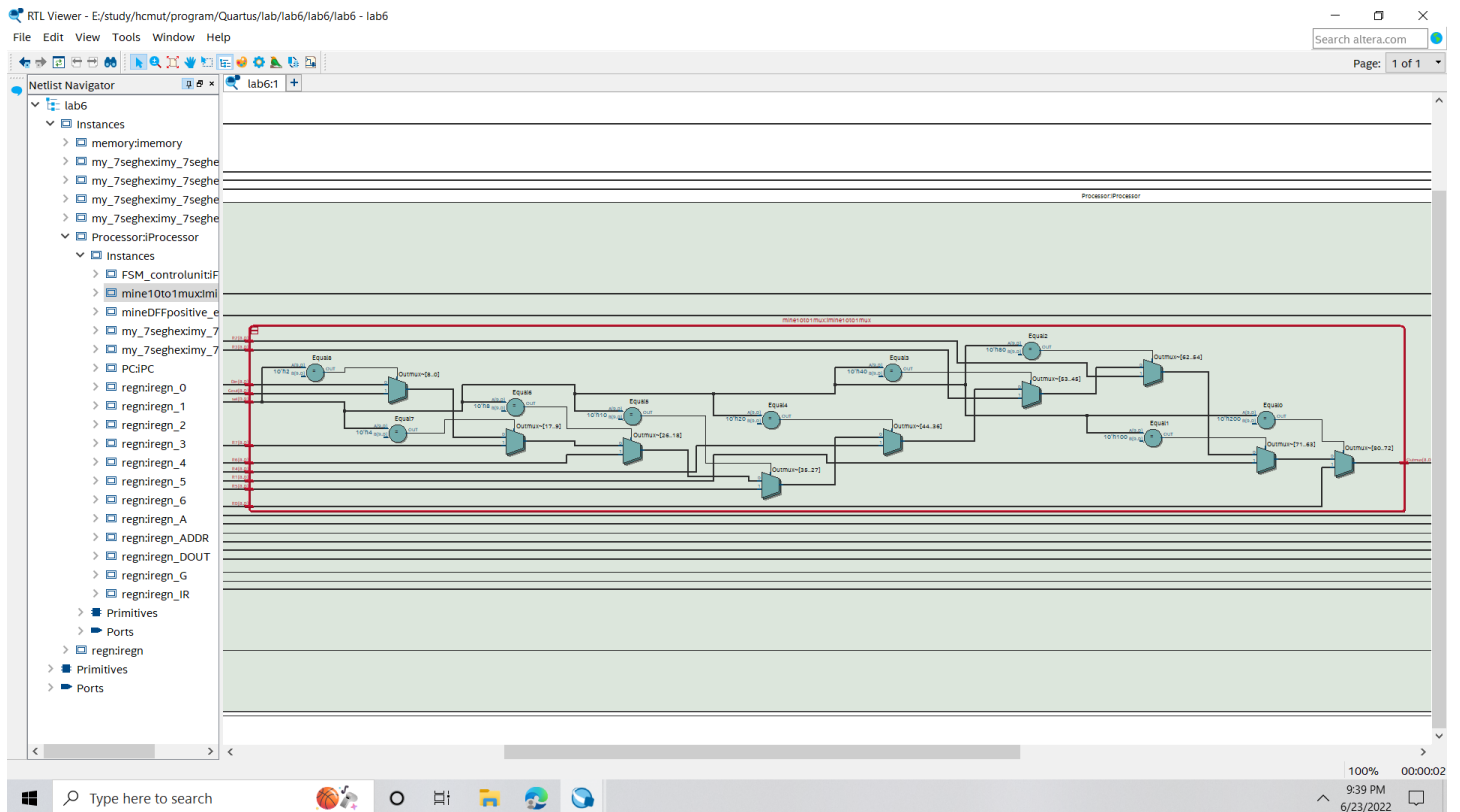


6) Memory:

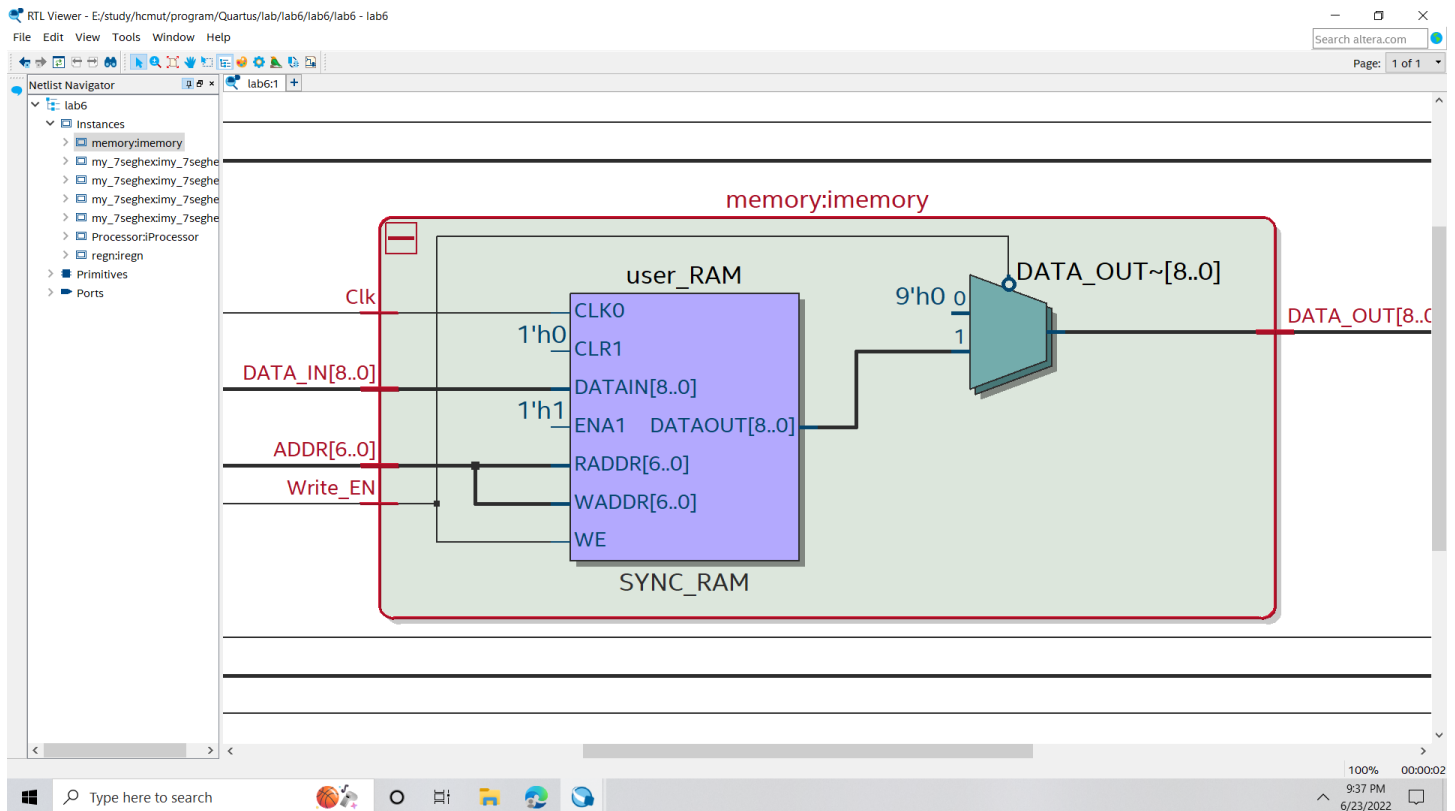

7) FSM control unit:

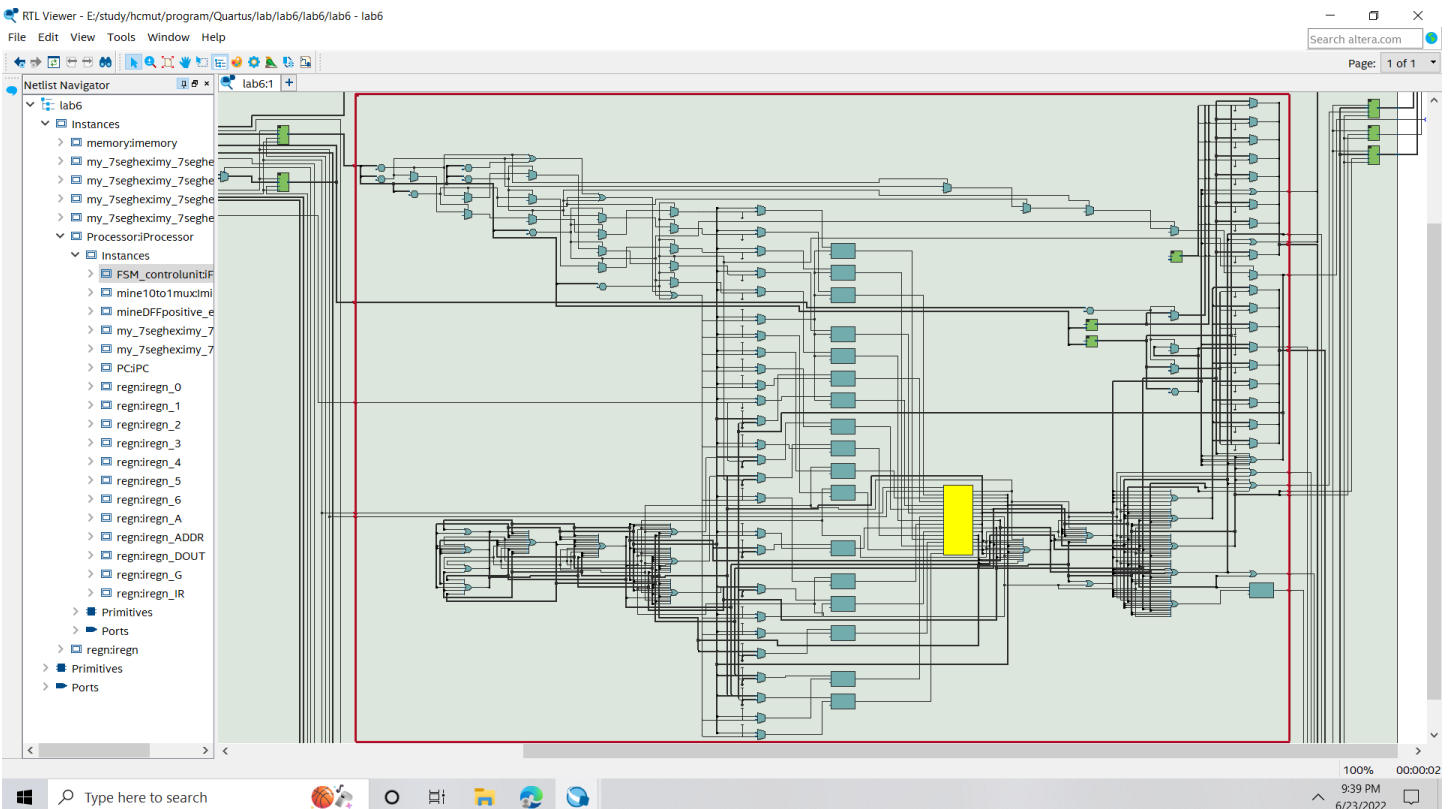

8) Processor :

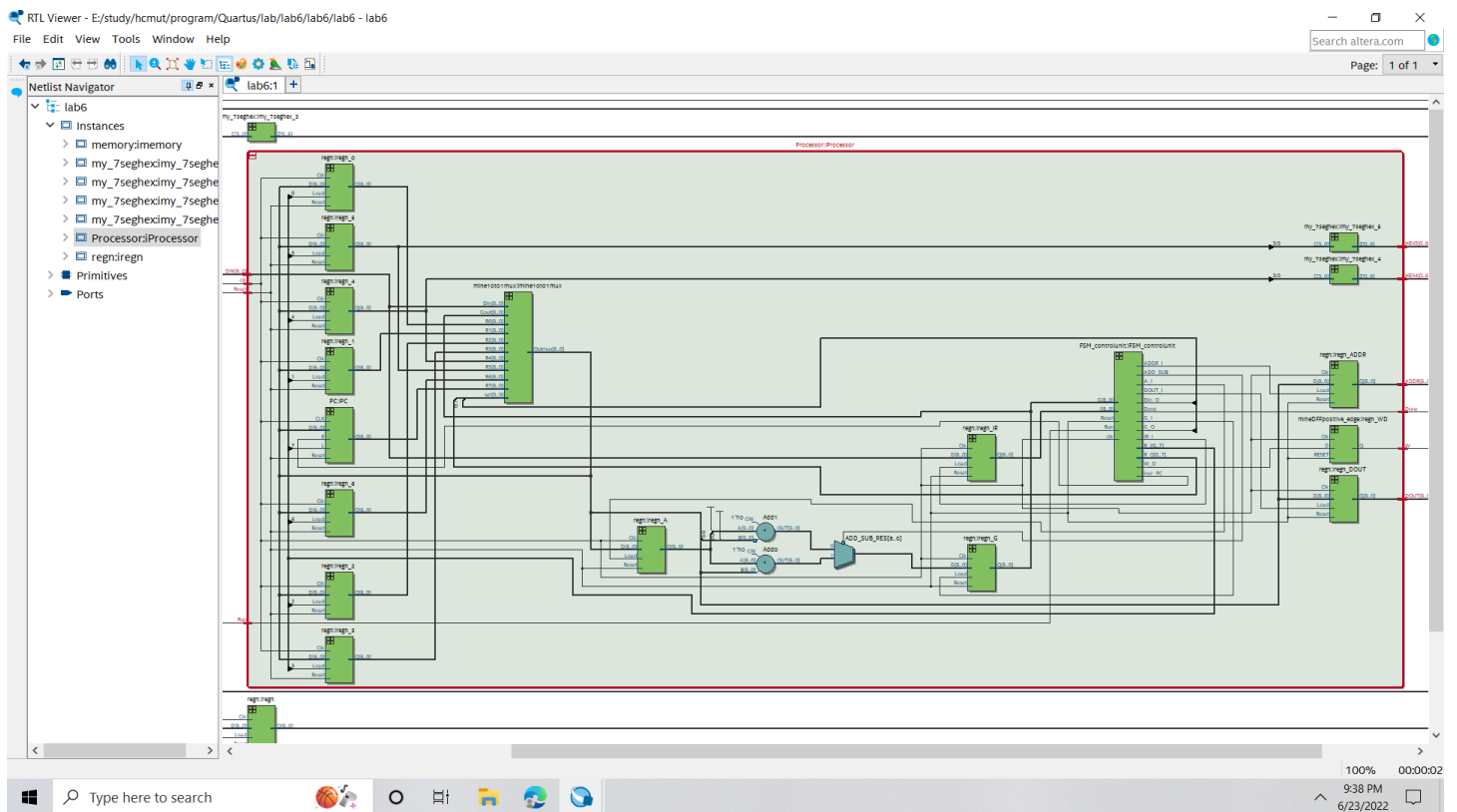

9) Overall LAB6:

